

P6 AUV

→ hard bugs
Bug 9

→ AUV was ^{easy}
TB's were hard

Fix Website
Dates

→ dont use # delays
in your comb logic

ENGR 210 / CSCI B441

Latches + Flip Flops

Andrew Lukefahr

Announcements

- P7 Saturating Counter is out
- P8 – Elevator Controller is out
 - This one is hard.

P7 pushed back a week

* P9 SPI is out

* Wednesday is Exam Review

UPDATE: ‘wire’ vs ‘logic’

SystemVerilog (NEW) Rules:
Just use ‘logic’*

* **EXCEPT**

logic foo = a & b; **(BAD - Initial values of a & b only)**

wire foo = a & b; **(OK)**

logic foo;
assign foo = a & b; **(OK)**

always_comb with case

```
module decoder (
    input [1:0] sel,
    output logic [3:0] out
);

always_comb begin
    out = 4'b0000; //default
    case(sel)
        2'b00: out=4'b0001;
        2'b01: out=4'b0010;
        2'b10: out=4'b0100;
                                // what about sel==2'b11?
    endcase
end

endmodule
```

Always specify
defaults for
always_comb!

Always specify defaults for
`always_comb`!

Always specify
defaults for
always_comb!

Combinational Logic

- Not or time
- a "combination" of inputs
- And/Or/NOT
- Output is combination of inputs

SEQUENTIAL LOGIC

DFF: Store
a value

- Sequence / time
- Output is combination of
current inputs and past
inputs


Sequential vs. Combinational

- Combinational Logic
 - The output is a combination of the **current inputs only**
- Sequential Logic
 - The output is a combination of the **current and past inputs**

SR Latch

<u>NOR</u>		
A	B	T
0	0	1
0	1	0
1	0	0
1	1	0

"Set-Reset Latch"

 

$$\text{pink} = 1$$

$$\text{cyan} = 0$$

<u>reset</u>	<u>Set</u>
1	0
0	0
0	1
0	0


<u>Q</u>	<u>\bar{Q}</u>
0	1
0	1
1	0
0	0

same inputs
different outputs

SR Latch w/ S=1 & R=1

Don't do this!

 = 1
 = 0


 


<u>Set</u>	<u>reset</u>	<u>Q</u>	<u>Q̄</u>
1	1	0	0

0 0

0,1,0,1,0,1,0,1,...

SR Latch w/NAND gates

  


→ better setup for ~~⇒~~ Flip-Flops

→ easier for me to draw

SR Latch with Enable

 Prevent changes in S & R from changing circuit output




S	R	E	Q	\bar{Q}
x	x	0	Q	\bar{Q}
1	0	1	1	0
0	1	1	0	1

* assume
no $S=1$
 $r=1$

D-Latch


"Data Latch"

 

D-Latch

= 1

= 0

 


D	en	<u>Q</u>	<u>Q</u>
-	0	0	1
1	1	1	0
0	1	0	1


Inputs to D Latches

Output Follows Input when Enable=1


Input D

 

enable

 

output Q

 


\bar{Q}


opposite of Q ... skip

Inputs to D Latches


Output Follows Input when Enable=1

 

Glitches

 


 
- Assume 10ps / gate.
- A=1, C=1, B falls
- What is F?



Glitch

- Unintended short errors in Boolean logic
- Caused by imbalance in gate delays

Glitches on D-Latches

  

What's wrong here?


```
logic x, y, z;  
logic foo, bar ;  
  
always_comb begin  
    if (x) foo = y & z;  
    if (x) bar = y | z;  
end
```

No default Case

Inferred Latches

```
logic x, y, z;  
logic foo, bar ;
```


Vulnerable
to a glitch →
~~Not~~

 

```
always_comb begin  
    if (x) enable a foo = y & z; //bad:  
    if (x) bar = y | z; // what if ~x?  
end
```

Defaults

```
wire x,y,z;  
logic foo, bar ;  
  
always_comb begin  
    foo = x; bar = x; //good: defaults  
    if (x) foo = y & z; //  
    if (x) bar = y | z ; //  
end
```

 


What if $x == 0$? $\text{foo} = \text{bar} = x!$

Always specify defaults for `always_comb`!


Always specify
defaults for
always_comb!

D Flip-Flop

 


Levels vs. Edges


D Flip-Flop vs. D Latch

 

 
The " $>$ " symbol tells you
it is Flip-Flop



D Flip-Flop vs. D Latch

 

 the " > " symbol tells you
it is Flip-Flop



D Flip-Flop in Verilog

```
module d_ff (
    input d,          //data
    input en,         //enable
    output logic q   //always block
);

    always_ff@(posedge en) //positive edge of enable
begin
    q <= d; //non-blocking assign
end

endmodule
```

D Flip-Flop w/ Clock

```
module d_ff (
    input d,          //data
    input clk,        //clock
    output logic q    //always block
);

    always_ff@(posedge clk)
    begin
        q <= d; //non-blocking assign
    end

endmodule
```

Blocking vs. NonBlocking Assignments



- Blocking Assignments (`=` in Verilog)
 - Execute in the order they are listed in a sequential block;
 - Upon execution, they immediately update the result of the assignment before the next statement can be executed.

LHS RHS
 $x \Leftarrow 2$

Blocking vs. NonBlocking Assignments

- Non-blocking assignments (\Leftarrow in Verilog):

- Execute concurrently
- Evaluate the expression of **all right-hand sides of each statement** in the list of statements **before assigning the left-hand sides**.
- Consequently, there is no interaction between the result of any assignment and the evaluation of an expression affecting another assignment.
- Nonblocking procedural assignments be used for all variables that are assigned a value within an edge-sensitive cyclic behavior.

  

Blocking vs. Non-Blocking Assignments

- ONLY USE BLOCKING ($=$) FOR COMBINATIONAL LOGIC
 - always_comb
- ONLY USE NON-BLOCKING ($<=$) FOR SEQUENTIAL LOGIC
 - always_ff
- Disregard what you see/find on the Internet!

BLOCKING (=) FOR

always_comb

NON-BLOCKING (<=) for

always_ff

D-FlipFlop w/Clock


```
module d_ff (
    input d,          //data
    input clk,        //clock
    output logic q    //in always block
) ;  
  
    always_ff @ (posedge clk)
begin
    q <= d; //non-blocking assign
end  
endmodule
```

What is q before posedge clk?

D-FF's with Reset

- Two different ways to build in a reset
 - Synchronous
 - Asynchronous


Verilog models of D flip-flop

 

Edge triggered D flip-flop:

```
logic Q;  
always_ff @ (posedge clk)  
    Q <= D;
```


No reset
ff

 

Edge triggered, asynchronous reset D flip-flop:

```
logic Q;  
always_ff @ (posedge clk, negedge rst)  
    if (~rst) Q <= 1'b0; //asynch. reset  
    else Q <= D;
```

Not used
in class

 

Edge triggered, synchronous reset, clock enable D flip-flop: C

```
logic Q;  
always_ff @ (posedge clk)  
    if (reset) Q <= 1'b0; // synch. reset  
    else Q <= d;
```

D-FlipFlop w/Reset

```
module d_ff (
    input d,                      //data
    input clk,                     //clock
    input rst,                  //reset
    output logic q                //output
);

    always_ff @(posedge clk)
    begin
        if (rst) q <= 'h0;
        else q <= d;
    end

endmodule
```